Fossil-Free MIT | Solar USB Phone Charger SOP | February 27, 2014

Estimated time: 2 hours and 20 minutes

Tools and supplies: Soldering iron (flat and point tips), multimeter, bright lamp for testing, wire-strippers, scissors, needle-nose pliers, aluminum foil, hot glue gun

Ingredients: Silicon solar cells (6, 2"x3"), tabbing wire (\sim 5" of wide, \sim 32" of narrow), solder (fine and thick), wire (solid-core, \sim 20 AWG, \sim 6" each of red and black is preferable), voltage step-up converter (\sim 3V input, 5V output) with USB female output (<u>example</u>), acrylic sheets (2, 7"x8", UV-resistant), hot glue sticks

Output: USB out, ~5V/1.5A under peak sunlight (standard iPhone charger is 5V/1A)

Safety considerations

- Never work alone!
- Never rush. Think and work deliberately.
- Be careful not to touch the soldering iron except on the handle. It will be hot. Very hot.
- Don't pick up any equipment by the electrical cord.
- Remove conductive metal jewelry and watches prior to working with exposed circuits.
- Make sure your hands are dry before using any electrical equipment.
- If anything seems unsafe or you're not sure what to do next, stop and ask for help.

Instructions

At steps with asterisks (***), please have a volunteer check your progress before proceeding.

(1) Connect 6 solar cells in series to get ~3V output (~80 minutes)

- (a) ***Choose 6 2"x3" cells: Make sure each set of 3 has the wafer corner cut in the same orientation
- (b) Prepare 8 tabs—strips of narrow tabbing wire (Ag-plated Cu)—each a bit longer than 4"
- (c) Attach a tab to the back side of each of the 6 cells
 - (i) Solder 1 tab to the back (gray) side of each cell, starting at one end of the tabbing wire (should have just over 2" hanging off the edge of each cell)
 - (ii) Apply flux to the silver contact (white strip) using flux pen before soldering
 - (iii) Test the power output of each individual cell using a multimeter
 - (1) $2'' \times 3'' = 5 \text{cm} \times 7.5 \text{cm} = 37.5 \text{cm}^2 \times 100 \text{mW/cm}^2 \times 10\% \text{ PCE} = -375 \text{mW}_p$
 - (2) Under bright sunlight, you should measure an output voltage of ~0.5V and output current of ~750mA
 - (3) Under a lamp in the lab, you may see much a lower current (100-300mA)
- (d) Cover the back side of each cell with transparent packing tape (just under 2" wide) for extra mechanical support on the tabs
- (e) Make 2 series-connected strings with 3 cells each
 - (i) Solder the overhanging tab from the back side of one cell (V+) onto the front side of the next (V-)
 - (ii) ***Check the order of the 3-cell strings for proper matching with the step-up polarity
 - (iii) Solder a narrow tab onto each of the two cells that have an untabbed side
- (f) Connect the 2 strings in series, side-by-side (in U-shape), using extra-wide tabbing wire
 - (i) Fold the wide tabbing wire over the leads at the ends and use thick solder to secure them together
- (g) ***Illuminate the cells and test the output voltage and current of the complete string using a multimeter: Should be \geq 3V at open circuit

Fossil-Free MIT | Solar USB Phone Charger SOP | February 27, 2014

- (i) When testing voltage, make sure not to short device through underlying Al foil
- (ii) If illumination is not uniform, output current will be lower than expected (below 100mA)
- (iii) Note the polarity of the string! Which end is positive?

(2) Connect the output of the PV string to the input of the step-up converter (~20 minutes)

- (a) Cut and strip ends of $\sim 6"$ long red and black wires
- (b) Solder red and black wires onto V+ and V- pins of step-up converter
- (c) ***Solder the free end of the red wire (from V+) to the positive end of the cell string
- (d) Solder the free end of the black wire (from V-) to the negative end of the cell string
- (e) ***Illuminate the module and test the voltage output of the step-up converter with a multimeter: You should measure clean 5V between V+ and GND, 2V between D- and GND, 2.7V between D+ and GND

(3) Encapsulate the entire PV string to complete the module (~40 minutes)

- (a) Cut acrylic sheets into 2 rectangles ($\sim 7"x8"$)
- (b) Place the cells face up onto one sheet with output wires extending out from shorter edge
- (c) ***Check that the second sheet lies flat on top and will not crack the cells when applied (no protruding high-stress points)
- (d) Use hot glue to secure key joints to the bottom acrylic sheet: mid-string connection (should be taped already), V+ and V- PV-wire joints, V+ and V- wires
- (e) Apply hot glue around the edges of the bottom sheet, then quickly place and align the top sheet
- (f) Fill in all the gaps between the sheets and seal all edges with hot glue
- (g) Attach the step-up converter to the top corner of the module using hot glue
- (h) *******Blanket all wires and step-up converter with hot glue, making sure not to shade any of the cells

(4) Solarize!

